

# The Valve Wizard

How to design valve guitar amplifiers!

[Home](#)

## Graphical Power Supply Design

This tutorial presents an easy way to predict the precise DC output voltage you will get from a particular power transformer and reservoir capacitor (assuming you actually have the transformer available to measure), when delivering a certain current to the load. The peak and RMS ripple current can also be predicted fairly accurately.

We will start with a [bridge rectifier as it is conceptually simpler than the two-phase](#) type. As shown in the diagram on the right, the transformer can be represented as a single source resistance,  $R_s$ , while the amplifier circuit (or whatever happens to be sucking current from the reservoir capacitor) can be represented as a load resistance,  $R_l$ . The reservoir capacitor is the dividing point between these two things- it is here that the behaviour of the circuit changes from short pulses of current, to smooth steady current. It doesn't matter which pair of diodes happen to be conducting, the current flows in  $R_s$  and  $R_l$  just the same on either cycle.

The source resistance is equal to the resistance of the secondary coil, plus the resistance of the primary coil when 'reflected' to the secondary:  
 $R_s = R_{sec} + R_{pri}/(V_{pri}/V_{sec})^2$   
Where:  
 $R_{sec}$  = measured resistance of the secondary winding.  
 $R_{pri}$  = measured resistance of the primary winding.  
 $V_{pri}$  = RMS primary voltage (e.g., mains voltage).  
 $V_{sec}$  = RMS secondary voltage measured with **no load**.

The amplifier circuit (or whatever happens to be draining current from the reservoir capacitor) can be represented as a single load resistance,  $R_l$ . This can be estimated simply as:  
 $R_l = V_{dc} / I_{load}$   
Where:  
 $V_{dc}$  = DC supply voltage after rectification (i.e., the voltage across the reservoir capacitor).  
 $I_{load}$  = average DC current demanded by the amplifier circuit.

If the amplifier runs in class A then its current demand does not change much with drive level, so as far as the power supply is concerned it looks like a constant resistance. A class AB amp, on the other hand, will demand less current at idle than at full drive, so its apparant resistance is not constant. Therefore, when estimating the load resistance, use whichever level of current you are more interested in. If you're really keen you could do two calculations, one for idle, one for full drive, so with the following method you could accurately predict the amount of voltage sag you will get under sustained overdrive...  
Of course, to find the load resistance we need first to *esimate* what the DC supply voltage will be. If the circuit were ideal the capacitor would charge up to the peak AC voltage, or  $V_{rms} \cdot \sqrt{2}$ . This should be close enough as most amplifiers will adjust their idle current to suit the supply voltage anyway, so they are more-or-less resistive.

Now, you might think that since  $R_s$  and  $R_l$  for a potential divider we could find the DC output voltage simply by taking the peak AC voltage and multiplying by the usual formula for a potential divider:  $R_s/(R_s+R_l)$ . However, that won't work here because this is a *non-linear* circuit. Trying to solve non-linear circuit problems with pure maths is tedious, and sometimes even impossible, but we can use a graphical technique instead:

Assuming we have measured the transformer voltage and resistances, estimated the load resistance, and chosen a value of reservoir capacitance, then it is easy to predict the DC output voltage of the power supply using the graph on the right.

First calculate the value of  $f \cdot C \cdot R_l$ , where  $f$  is you mains frequency (50 or 60Hz). Then calculate the ratio  $R_s/R_l$ . The graph then shows what the DC output voltage will be, compared with the AC transformer voltage. (Your value of  $f \cdot C \cdot R_l$  probably won't correspond exactly to one of the curves shown, so just estimate its position compared with the others. Note that there isn't much change once you get above  $f \cdot C \cdot R_l = 2$ ).

For example, suppose we are building a power supply using a "200V" transformer, but with no load we find that it actually measures:  
 $V_{sec} = 220V_{rms}$   
 $R_{pri} = 70 \text{ ohms}$   
 $R_{sec} = 240 \text{ ohms}$   
And also:  
 $V_{pri} \text{ (mains voltage)} = 230V$   
Mains frequency  $f = 50\text{Hz}$

We estimate that it ought to provide roughly  $200 \cdot \sqrt{2} = 282V_{dc}$  after rectification. It will be used to power a small amplifier that will consume about 40mA. From this we estimate the load resistance to be:  
 $R_l = 282 / 0.04 = 7050 \text{ ohms}$ .

The source resistance  $R_s$  is:  
 $R_s = 240 + 70/(230/220)^2 = 304 \text{ ohms}$ .  
So the ratio  $R_s / R_l$  is:  
 $R_s/R_l = 304/7050 = 0.043$


We decide to use a 100uF resevoir capacitor, so altogether:  
 $f \cdot C \cdot R_l = 35$

Reading off the graph above (shown by the dashed lines) we see the DC output voltage will be about 116% of the measured RMS voltage, or:  
 $220V_{rms} \cdot 116/100\% = 255V_{dc}$ .  
This is less than our simple estimate of 282V because of the voltage lost across the source resistance. Maybe this would cause us to re-think the amplifier design, or maybe we would consider it OK.

Something else we might be interested in is the ripple current that flows around the transformer and rectifier, which can be estimated using the graph on the right. The *average* ripple current is the same as the DC load current, so the diodes must be rated for this much current, but the RMS and peak values of the ripple current will be higher.

Using the previous example, if the amplifier load current is 40mA then the RMS ripple current is indicated to be about 1.8 times the load current, or  $40mA \cdot 1.8 = 72mA$ . The transformer needs to be rated to handle at least this much current.

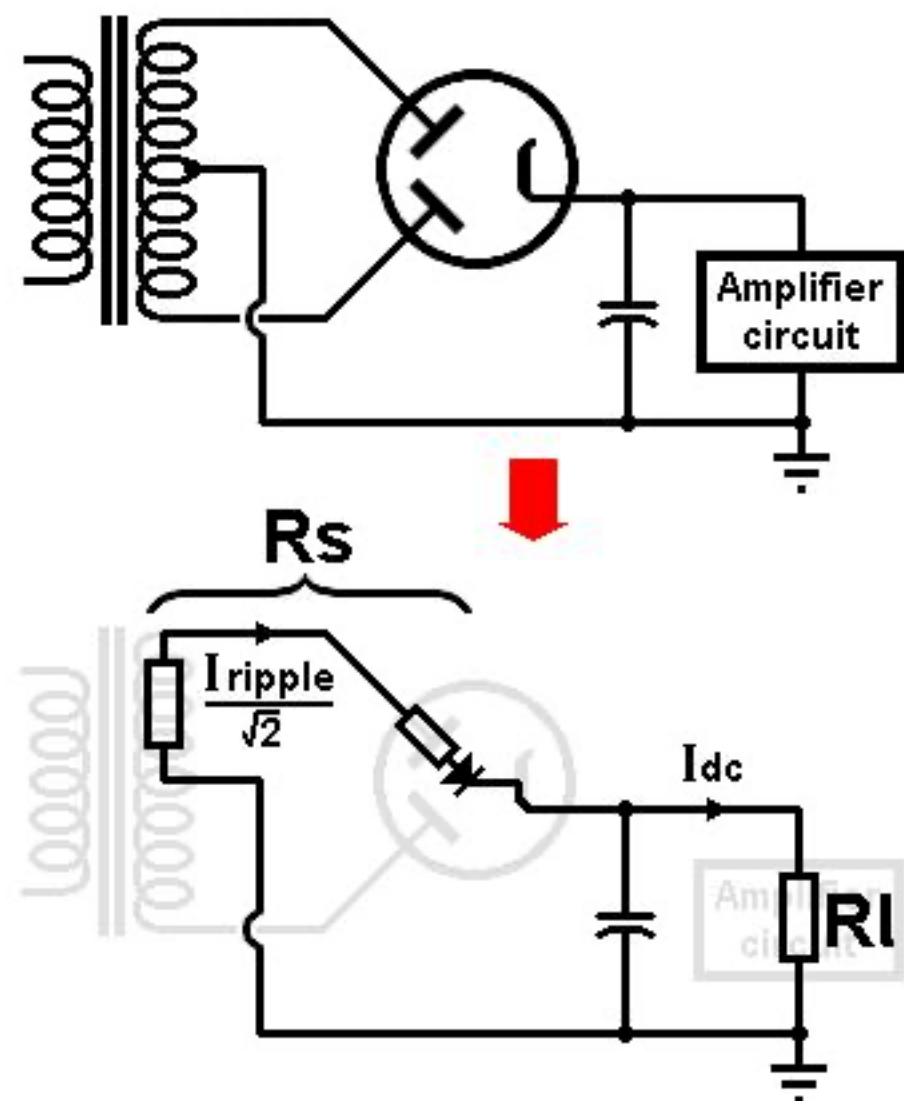The graph also shows the peak ripple current will be about 4.1 times the load current, or  $40mA \cdot 4.1 = 164mA$ .  
Valve rectifiers often have a maximum limit for peak ripple current, but silicon rectifiers can handle any likely situation as long as their average current rating is sufficient.



For a [two-phase](#) rectifier the voltages can be predicted in exactly the same way as above, except that we only need to consider *half* the transformer's secondary winding, as indicated by the diagram on the left. Also, if a valve rectifier is used, then its internal anode resistance also forms part of the total source resistance  $R_s$ , as shown. This is not constant, so just use a ball-park average. This can be obtained from the valve data sheet (for a GZ34 it is about 50 ohms).

Finding the ripple current can also be done in the same way, except the graph above indicates the *total* ripple current flowing from the rectifier into the reservoir capacitor. This total current is shared between the two halves of the transformer winding, but it is NOT simply half the total value. In fact, the current in each 'leg' of the transformer (and therefore in each valve diode- there are two in the bottle, remember) is  $1/\sqrt{2}$  or about 70% of the total. This is why two-phase transformers need thicker wire than single-winding transformers of equivalent rating.

If the valve data sheet indicates that limiting resistors are required, then we can use the RMS ripple current to work out how much power they will dissipate, since  $P = I^2 R$  (these resistors add to  $R_s$  too, of course).  
For example, if we are using 100 ohm resistors on each anode, and the graph happens to indicate the *total* RMS ripple current to be 100mA, then the RMS ripple current in each leg of the transformer will be  $100/\sqrt{2} = 71mA$ , so each resistor will dissapate  $100^2 \cdot 0.071^2 = 0.5W$ . Thus we might choose 2W resistors to be really safe.

