

LIFE ON THE ROAD



TYMPHANY | TYMPHANY AUTOMOTIVE GROUP | Peerless



(https://audioxpress.com/waitress/follow/454)

SHARE

preamplifier (https://audioxpress.com/tags/preamplifier)

DIY project (https://audioxpress.com/tags/DIY-project) Show more (6)

by Mike Danbury (/authors/23490/mike-danbury) on Project Articles (/categories/project-articles)

IIN Article

Preamp Muting Circuit

O February 2 2018, 02:00

Oftentimes a muting circuit for the output of a preamp is left out of DIY applications as an unnecessary or annoying part of the project. This is usually due to the lack of awareness that a simple circuit can perform such a duty. Anyone who occasionally forgets to turn the power amp on last, or switch it off first, endures the annoying thumps and noises that often occur from the preamp upon power cycling. The schematic for a simple circuit for preamp muting appears in Fig. 1.



Preamp Muting Circuit

The Audio Voice

App Sigtiments

(http://visitor.r20.consta/https://audioxpress.com/categories/app llr=4tkwpoeab&p=oi&m=1104292817535&sit=upajn4wfb&f=b458eb46-a11d-4ae1-aa30-4a1e_190008eb

(https://audioxpress.com/categories/blo

(https://audioxpress.com/categories/elec

Industry News

(https://audioxpress.com/categories/ind news)

<u>Interviews</u>

(https://audioxpress.com/categories/inte

Magazine Articles

(https://audioxpress.com/categories/ma; articles)

Magazine News

(https://audioxpress.com/categories/mag news)

Product News

(https://audioxpress.com/categories/pro news)

Project Articles

(https://audioxpress.com/categories/pro articles)

Sponsored

(https://audioxpress.com/categories/spo

Theory Articles

(https://audioxpress.com/categories/the articles)

Voice Coil Test Bench

(https://audioxpress.com/categories/vctestbench)



(https://audioxpress.com/waitress.

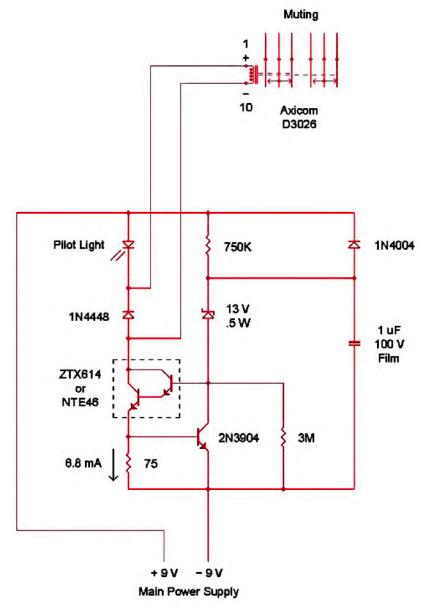


Figure 1: Schematic of a simple circuit for preamp muting.

The Circuit

The circuit draws its power from the raw supply rails of the existing preamp, drawing only 7mA of current; you can adjust it for a range of operating voltages by simply changing the value of the zener diode. No connection to the preamp's GND is needed, so there's no risk of any annoying ground currents developing. With the values given in the schematic, the turn-on delay is around 1.5 seconds. The turn-off delay depends on the rate of power supply collapse at power-off, because the $1\mu F$ timing capacitor discharges through the 1N4004 diode back into the main supply.

This raises the one word of caution about using such a circuit: The power supply must have sufficiently large power supply capacitors to allow the muting circuit time to switch off before the preamp starts to exhibit anomalous behavior, typically around 50mS minimum. This holds true for any muting circuit to function properly, though.


The $\pm 9V$ rails represent about the minimum operating voltage for the circuit with the pilot light in series with the relay. If you replace the pilot light with a jumper and change the zener to 10V, the minimum supply rails will be around $\pm 7.5V$. The maximum supply rails are around $\pm 45V$ as you approach the breakdown voltage and power limits of the Darlington. You should select the zener to be around 5 or 6V less than the expected operating voltage, although at higher voltages you can use a greater difference.



(https://audioxpress.com/waitress/



(https://audioxpress.com/waitress.

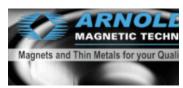

(https://audioxpress.com/waitress.



(https://audioxpress.com/waitress.



(https://audioxpress.com/waitress.

The muting relay itself has a DPDT set of contacts (and is available from Mouser Electronics), so you can choose to implement either a series (normally open) or shunt to ground (normally closed) muting scheme (Fig. 2).

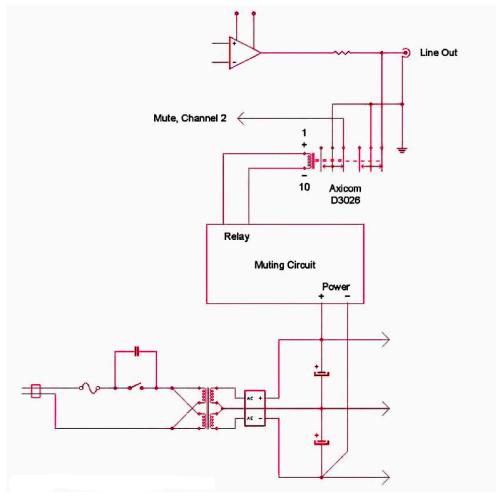


Figure 2: Example of a shunt muting configuration.


With the exception of mounting the 1N4448 diode close to the relay coil, layout and construction are not critical. In the prototype I mounted the circuit with the pilot light at the front panel and hot-glued the relay to the rear panel using the shunt muting scheme across the RCA jacks. **aX**

This article was originally published in audioXpress, March 2010

« BACK SHARE

RELATED ITEMS



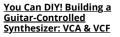




You Can DIY! Building a Guitar-Controlled Synthesizer: Input Section



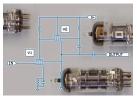You Can DIY! Building a Guitar-Controlled Synthesizer: LFO and



You Can DIY! Meet the Pentriode

(https://audioxpress.com/(https://audioxpress.com/(https://audioxpress.com/(https://audioxpress.com/(https://audioxpress.com/can-diy-building-a-guitar-a-guitar-a



(https://audioxpr


Industry Events

Current issue



audioXpress Decemb 2022

 Inside This Issue (https://audioxpress.c

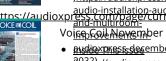

<u>ANZZ}</u>://audioxpress.c ■ <u>Supplemental Materia</u>

(https://audioxpress-

Trending



October 18, 2022 NAD Electronics Announces 50th Anniversary Limited

(https://audioxpress.com/news/nacelectronics-announces-3050-lestereophonic-amplifier-50th-annivelimited-edition/) SHARE / READ MORE...

(HTTPS://AUDIOXPRESS.CO ELECTRONICS-ANNOUNCE: LE-STEREOPHONIC-AMPLIF ANNIVERSARY-LIMITED-EDI



October 18, 2022 SEAS and Merry Electronics Annound Launch of New SEAS

(https://audioxpress.com/news/sea merry-electronics-announce-the-lau of-new-seas-orbit-speaker-series/)

SHARE / READ MORE...
(HTTPS://AUDIOXPRESS.CO
AND-MERRY-ELECTRONICS
ANNOUNCE-THE-LAUNCHSEAS-ORBIT-SPEAKER-SERII

controlled-synthesizer-						<u>pentriode)</u>	
<u>vca-vcf)</u>		input-section	<u>ı-pick-</u>	<u>lfo-and-adsr</u>)			READ MORE
	READ MORE	<u>detector)</u>			READ MORE		(HTTPS://AUDIOXPRI
	(HTTPS://AUDIOXPR		READ MORE		(HTTPS://AUDIOXPR		CAN-DIY-MEET-THE-
	CAN-DIY-BUILDING-		(HTTPS://AUDIOXPRI		CAN-DIY-BUILDING-		PENTRIODE)
	A-GUITAR-		CAN-DIY-BUILDING-		A-GUITAR-		
	CONTROLLED-		A-GUITAR-		CONTROLLED-		
	SYNTHESIZER-VCA-		CONTROLLED-		SYNTHESIZER-LFO-		
	VCF)		SYNTHESIZER-		AND-ADSR)		
			INPUT-SECTION-				
			PICK-DETECTOR)				



November 2, 2022

Patent Review: Low Loudspeaker Device

(https://audioxpress.com/article/pa review-low-profile-loudspeaker-dev

> SHARE / READ MORE... (HTTPS://AUDIOXPRESS.CO REVIEW-LOW-PROFILE-LOUDSPEAKER-DEVICE/)



November 1, 2022 **New COMSOL Multi** Version 6.1 Reinforc

(https://audioxpress.com/news/nev comsol-version-6-1-of-comsolmultiphysics-reinforces-transducerdesign-for-audio-products/)

> SHARE / READ MORE... (HTTPS://AUDIOXPRESS.CO COMSOL-VERSION-6-1-OF-MULTIPHYSICS-REINFORCE TRANSDUCER-DESIGN-FOR PRODUCTS/)



October 25, 2022

GaN Systems Extend Class D Audio Soluti With New Amplifier

(https://audioxpress.com/news/gan systems-extends-class-d-audio-solu with-new-amplifier-modules-and-bo converters/) SHARE / READ MORE...

(HTTPS://AUDIOXPRESS.CO SYSTEMS-EXTENDS-CLASS-I SOLUTIONS-WITH-NEW-AM MODULES-AND-BOOST-CONVERTERS/)

FOLLOW US

 $\underline{ VOICE} \underline{ \hspace{-0.05cm} \hspace{-0.0$





audioxpress Media kihttps://audioxpress.com/page/Loudspeakerr.Industry-Sourcebook-MediatKikihtml)

f (http://www.facebook.com/audioxpresscommunity) **②** (https://twitter.com/audioXP_editor) **❷** (mailto:webmaster@audioxpress.com)

Disclaimer (/page/Disclaimer.html) | Terms and Conditions (/page/General-Terms-and-Conditions.html) | Terms of Use (/page/Terms-of-us